

Verilog Design Report: Convolution, Adder, and Ripple Carry Adder

Dhawal(EE24BTECH11015)

April 23, 2025

1 Question 1: 8-Element Vector Convolution Module

1.1 Detailed Approach

1. The convolution module computes the discrete linear convolution of two 8-element vectors.
2. Input vectors x and h are each 4-bit wide (8 elements total).
3. The output has 16 elements (8+8-1) due to convolution properties.
4. Each output element $y[n]$ is calculated as the sum of products of $x[k]$ and $h[n-k]$.
5. The implementation uses combinatorial logic with an always @(*) block.
6. Temporary 8-bit registers store intermediate results before truncation.
7. The design performs parallel multiplications and additions for each output tap.
8. Output is truncated to 4 bits by taking only the lower nibble of each result.
9. No pipelining is implemented - this is a purely combinatorial design.
10. The module demonstrates direct implementation of convolution formula without optimization.

1.2 Code Explanation

Key points about the implementation:

- Input vectors are split into individual 4-bit elements (x0-x7, h0-h7)
- 16 output elements (y0-y15) cover all possible convolution results
- Temporary 8-bit registers prevent overflow during intermediate calculations
- Combinatorial always block calculates all outputs simultaneously
- Each output is the sum of relevant input products
- Final assignments truncate results to 4 bits
- No clock or reset needed - pure combinational logic
- Simple direct implementation of convolution formula

Convolution Module Code

```
module convolution (
    input  [3:0] x0, x1, x2, x3, x4, x5, x6, x7,
    input  [3:0] h0, h1, h2, h3, h4, h5, h6, h7,
    output [3:0] y0, y1, y2, y3, y4, y5, y6, y7,
                y8, y9, y10, y11, y12, y13, y14, y15
);
    reg [7:0] temp0, temp1, temp2, temp3, temp4,
    temp5, temp6, temp7;
    reg [7:0] temp8, temp9, temp10, temp11,
    temp12, temp13, temp14, temp15;
```

```

always @(*) begin
    temp0 = (x0 * h0);
    temp1 = (x0 * h1) + (x1 * h0);
    temp2 = (x0 * h2) + (x1 * h1) + (x2 * h0);
    temp3 = (x0 * h3) + (x1 * h2) + (x2 * h1) + (x3 * h0);
    temp4 = (x0 * h4) + (x1 * h3) + (x2 * h2) + (x3 * h1) + (x4 * h0);
    temp5 = (x0 * h5) + (x1 * h4) + (x2 * h3) + (x3 * h2) + (x4 * h1)
    + (x5 * h0);
    temp6 = (x0 * h6) + (x1 * h5) + (x2 * h4) + (x3 * h3) + (x4 * h2)
    + (x5 * h1) + (x6 * h0);
    temp7 = (x0 * h7) + (x1 * h6) + (x2 * h5) + (x3 * h4) + (x4 * h3)
    + (x5 * h2) + (x6 * h1) + (x7 * h0);
    temp8 = (x1 * h7) + (x2 * h6) + (x3 * h5) + (x4 * h4) + (x5 * h3)
    + (x6 * h2) + (x7 * h1);
    temp9 = (x2 * h7) + (x3 * h6) + (x4 * h5) + (x5 * h4) + (x6 * h3)
    + (x7 * h2);
    temp10 = (x3 * h7) + (x4 * h6) + (x5 * h5) + (x6 * h4) + (x7 * h3);
    temp11 = (x4 * h7) + (x5 * h6) + (x6 * h5) + (x7 * h4);
    temp12 = (x5 * h7) + (x6 * h6) + (x7 * h5);
    temp13 = (x6 * h7) + (x7 * h6);
    temp14 = (x7 * h7);
    temp15 = 0;
end

assign y0 = temp0[3:0];
assign y1 = temp1[3:0];
assign y2 = temp2[3:0];
assign y3 = temp3[3:0];
assign y4 = temp4[3:0];
assign y5 = temp5[3:0];
assign y6 = temp6[3:0];
assign y7 = temp7[3:0];
assign y8 = temp8[3:0];
assign y9 = temp9[3:0];
assign y10 = temp10[3:0];
assign y11 = temp11[3:0];
assign y12 = temp12[3:0];
assign y13 = temp13[3:0];
assign y14 = temp14[3:0];
assign y15 = temp15[3:0];
endmodule

```

1.3 Testbench

Key testbench features:

- Tests three different input scenarios
- Includes basic, impulse, and max-value test cases
- Uses $\$display$ for test case identification
- Generates VCD file for waveform viewing
- 20ns delay between test cases
- Verifies correct convolution operation

```

`timescale 1ns/1ps

module tb_convolution_all;
    reg [3:0] x0, x1, x2, x3, x4, x5, x6, x7;
    reg [3:0] h0, h1, h2, h3, h4, h5, h6, h7;
    wire [3:0] y0, y1, y2, y3, y4, y5, y6, y7,
              y8, y9, y10, y11, y12, y13, y14, y15;

    convolution uut (
        x0, x1, x2, x3, x4, x5, x6, x7,
        h0, h1, h2, h3, h4, h5, h6, h7,
        y0, y1, y2, y3, y4, y5, y6, y7,
        y8, y9, y10, y11, y12, y13, y14, y15
    );

    initial begin
        $dumpfile("convolution_all.vcd");
        $dumpvars(0, tb_convolution_all);
    end

    initial begin
        // Test 1: Basic Increasing x, uniform h
        $display("Test 1: Basic Increasing x, uniform h");
        x0=1; x1=2; x2=3; x3=4; x4=0; x5=0; x6=0; x7=0;
        h0=1; h1=1; h2=1; h3=1; h4=0; h5=0; h6=0; h7=0;
        #20;

        // Test 2: Impulse x
        $display("Test 2: Impulse x");
        x0=1; x1=0; x2=0; x3=0; x4=0; x5=0; x6=0; x7=0;
        h0=1; h1=2; h2=3; h3=4; h4=0; h5=0; h6=0; h7=0;
        #20;

        // Test 3: Max Edge
        $display("Test 3: Max input values");
        x0=15; x1=15; x2=15; x3=15; x4=15; x5=15; x6=15; x7=15;
        h0=15; h1=15; h2=15; h3=15; h4=15; h5=15; h6=15; h7=15;
        #20;

        $display("Simulation complete");
        $finish;
    end
endmodule

```

1.4 Timing Diagram

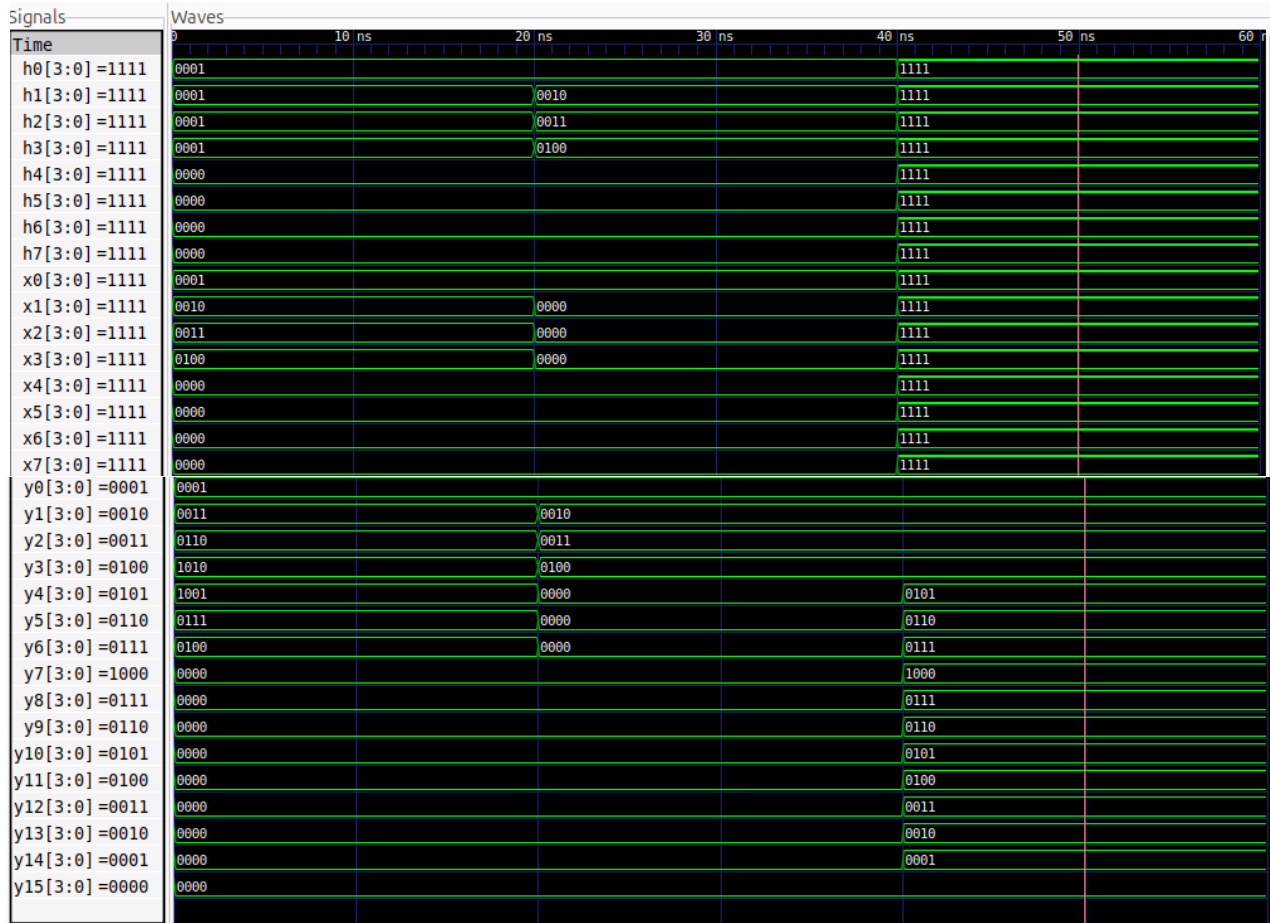


Figure 1: Timing diagram showing convolution outputs for different input patterns

2 Question 2: 8-bit Full Adder Using Loop Statements

2.1 Detailed Approach

1. The design implements an 8-bit adder using a generate loop.
2. It instantiates 8 full adder modules in a cascaded fashion.
3. The generate block creates a ripple-carry adder structure.
4. First full adder handles the carry-in input specially.
5. Subsequent adders connect to previous carry-out.
6. Uses a hierarchical design with a basic full adder module.
7. The loop variable 'i' creates unique instances for each bit.
8. Internal carry wires connect adjacent full adders.
9. Final carry-out comes from the last full adder.
10. Demonstrates parameterized design using Verilog generate.

2.2 Code Explanation

Key points about the implementation:

- Uses hierarchical design with 1-bit full adder module
- Generate loop creates 8 instances of full adder

- Special handling for first adder's carry-in
- Internal carry chain connects adjacent adders
- Clean separation of module definition and instantiation
- Demonstrates Verilog's generate construct
- Efficient parameterized design
- Easy to scale to different bit widths

8-bit Adder Module Code

```

module full_adder (
    input  a, b, cin ,
    output sum, cout
);
    assign sum = a ^ b ^ cin;
    assign cout = (a & b) | (b & cin) | (a & cin);
endmodule

module adder_8bit (
    input  [7:0] A, B,
    input    Cin ,
    output [7:0] Sum,
    output    Cout
);
    wire [7:0] carry;

    genvar i;
    generate
        for (i = 0; i < 8; i = i + 1) begin : full_adder_loop
            if (i == 0) begin
                full_adder FA (
                    .a(A[i]),
                    .b(B[i]),
                    .cin(Cin),
                    .sum(Sum[i]),
                    .cout(carry[i])
                );
            end else begin
                full_adder FA (
                    .a(A[i]),
                    .b(B[i]),
                    .cin(carry[i-1]),
                    .sum(Sum[i]),
                    .cout(carry[i])
                );
            end
        end
    endgenerate

    assign Cout = carry[7];
endmodule

```

2.3 Testbench

Key testbench features:

- Tests four different addition scenarios
- Includes basic, carry-in, and overflow cases

- Verifies both sum and carry-out outputs
- 10ns delay between test cases
- Uses binary literals for input values
- Clear display messages for each test

8-bit Adder Testbench

```

`timescale 1ns / 1ps

module tb_adder_8bit;
    reg [7:0] A, B;
    reg      Cin;
    wire [7:0] Sum;
    wire      Cout;

    adder_8bit uut (
        .A(A),
        .B(B),
        .Cin(Cin),
        .Sum(Sum),
        .Cout(Cout)
    );

    initial begin
        $dumpfile("adder_8bit.vcd");
        $dumpvars(0, tb_adder_8bit);

        // Test 1: Basic Addition
        A = 8'b00001111; B = 8'b00000001; Cin = 0; #10;

        // Test 2: With Carry-in
        A = 8'b11110000; B = 8'b00001111; Cin = 1; #10;

        // Test 3: Max values
        A = 8'b11111111; B = 8'b11111111; Cin = 0; #10;

        // Test 4: Random pattern
        A = 8'b10101010; B = 8'b01010101; Cin = 0; #10;

        $display("Simulation complete.");
        $finish;
    end
endmodule

```

2.4 Timing Diagram

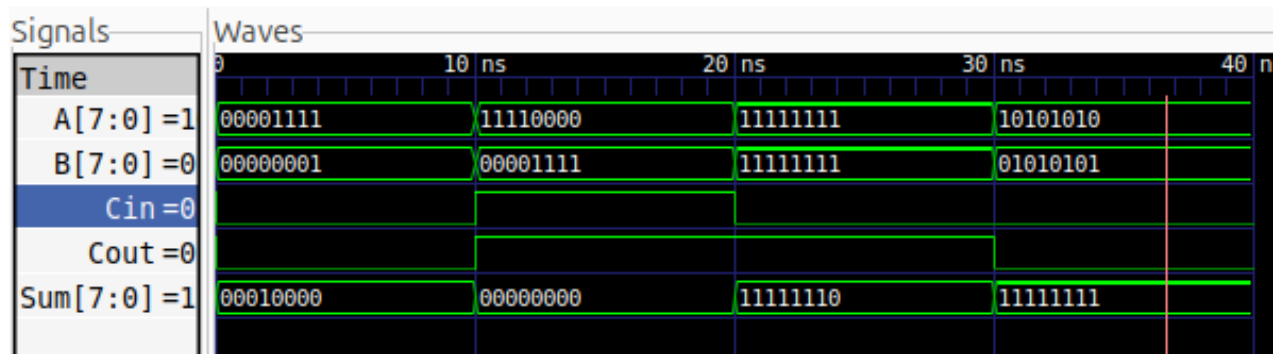


Figure 2: Timing diagram showing 8-bit adder operation with carry propagation

3 Question 3: 4-bit Ripple Carry Adder Using NAND Gates

3.1 Detailed Approach

1. Implements a 4-bit adder using only 2-input NAND gates.
2. Each NAND gate has 1ns propagation delay.
3. Hierarchical design with basic logic gates built from NANDs.
4. Includes NOT, AND, OR, and XOR implementations using NANDs.
5. Full adder constructed from these basic gates.
6. Ripple carry adder chains 4 full adders together.
7. Carry propagates through each stage sequentially.
8. Demonstrates universal gate implementation.
9. Shows gate-level design with precise timing.
10. Testbench verifies correct operation with timing checks.

3.2 Code Explanation

Key points about the implementation:

- All logic gates derived from NAND gates
- Precise 1ns delay per NAND gate
- Hierarchical design from basic gates to full adder
- Ripple carry structure with explicit carry propagation
- Demonstrates universal gate property of NAND
- Gate-level implementation shows actual hardware
- Clear separation of different logic functions
- Includes all necessary intermediate wires

NAND-based Adder Code

```
'timescale 1ns / 1ps

module nand2(input a, b, output y);
    assign #1 y = ~(a & b);
```

```

endmodule

module not_nand(input a, output y);
    nand2 n1(a, a, y);
endmodule

module and_nand(input a, b, output y);
    wire t;
    nand2 n1(a, b, t);
    nand2 n2(t, t, y);
endmodule

module or_nand(input a, b, output y);
    wire na, nb;
    not_nand n1(a, na);
    not_nand n2(b, nb);
    nand2 n3(na, nb, y);
endmodule

module xor_nand(input a, b, output y);
    wire t1, t2, t3;
    nand2 n1(a, b, t1);
    nand2 n2(a, t1, t2);
    nand2 n3(b, t1, t3);
    nand2 n4(t2, t3, y);
endmodule

module full_adder_nand(input a, b, cin, output sum, cout);
    wire axb, ab, bc, ac, t;
    xor_nand x1(a, b, axb);
    xor_nand x2(axb, cin, sum);
    and_nand a1(a, b, ab);
    and_nand a2(b, cin, bc);
    and_nand a3(a, cin, ac);
    or_nand o1(ab, bc, t);
    or_nand o2(t, ac, cout);
endmodule

module ripple_carry_adder_4bit(
    input  [3:0] A, B,
    input      Cin,
    output [3:0] Sum,
    output      Cout
);
    wire c1, c2, c3;

    full_adder_nand fa0(A[0], B[0], Cin, Sum[0], c1);
    full_adder_nand fa1(A[1], B[1], c1, Sum[1], c2);
    full_adder_nand fa2(A[2], B[2], c2, Sum[2], c3);
    full_adder_nand fa3(A[3], B[3], c3, Sum[3], Cout);
endmodule

```

3.3 Testbench

Key testbench features:

- Tests five different addition scenarios
- Includes overflow, simple, and random cases
- 100ns delay to observe gate delays

- Verifies correct timing behavior
- Tests all bits and carry chains
- Includes edge cases and typical patterns

NAND Adder Testbench

```

`timescale 1ns / 1ps

module tb_ripple_adder;
    reg [3:0] A, B;
    reg      Cin;
    wire [3:0] Sum;
    wire      Cout;

    ripple_carry_adder_4bit uut (
        .A(A), .B(B), .Cin(Cin),
        .Sum(Sum), .Cout(Cout)
    );
    initial begin
        $dumpfile("ripple_adder.vcd");
        $dumpvars(0, tb_ripple_adder);

        // Test 1: 15 + 15 + 1 = 31 (Overflow)
        A = 4'b1111; B = 4'b1111; Cin = 1; #100;

        // Test 2: 1 + 2 = 3
        A = 4'b0001; B = 4'b0010; Cin = 0; #100;

        // Test 3: Alternating bits with Cin
        A = 4'b1010; B = 4'b0101; Cin = 1; #100;

        // Test 4: All zeros
        A = 4'b0000; B = 4'b0000; Cin = 0; #100;

        // Test 5: Random mix
        A = 4'b1001; B = 4'b0110; Cin = 1; #100;
        $finish;
    end
endmodule

```

3.4 Timing Diagram

 


Figure 3: Timing diagram showing ripple carry propagation in 4-bit adder

<https://github.com/Dhawal24112006/EE1501.git>